

DESIGN OF HALF AND FULL ADDER

AIM:

To design and simulate half adder, full adder using basic gates and full adder using 2 half adders.

HALF ADDER USING BASIC GATES:

A logic circuit block used for adding two one-bit numbers or simply two bits is called as a half adder circuit. This circuit has two inputs which accept the two bits and two outputs, with one producing sum output and other produce carry output.


As we know that binary addition is commonly performed by Ex-OR gate, but for the first three rules, it performs the binary addition and when the two inputs are logic 1, it does not develop any carry.

To accomplish the binary addition with Ex-OR gate, there is need of additional circuitry to perform the carry operation. Hence, a half adder is formed by connecting AND gate to the input terminals of the Ex-OR gate so as to produce the carry.

$$\text{Sum } (\Sigma) = A \oplus B$$

$$\text{Carry Out (Co)} = A \cdot B$$

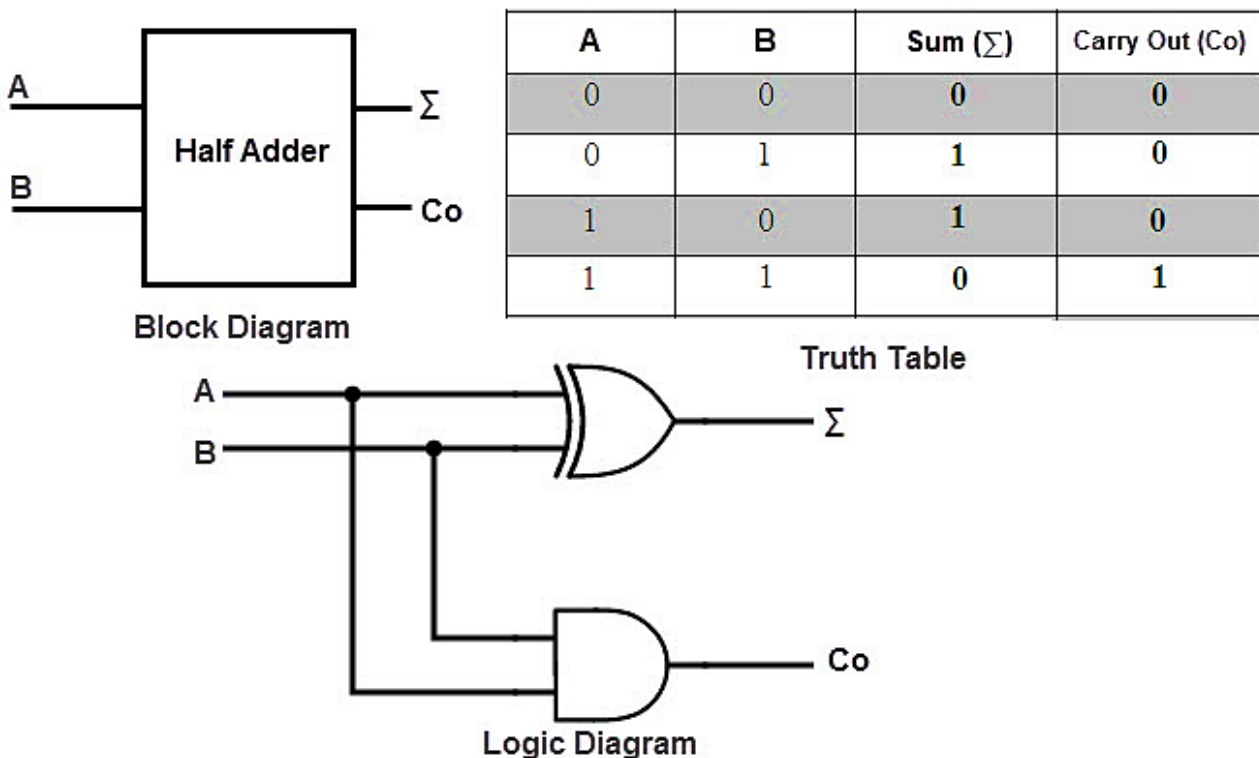The block diagram, circuit diagram and the truth table for half adder is given below:



The i/o ports needed to be declared for the formation of half adder is given below:


Port Name	INPUT/OUTPUT	Bus
A	In	No
B	In	No
Sum	Out	No
Cout	Out	No

NB: Use temporary variable where ever necessary.

FULL ADDER USING BASIC GATES:

Full adder is a digital circuit used to calculate the sum of three binary bits which is the main difference between full adder and half adder. Full adders are complex and difficult to implement when compared to half adders. The additional third bit is carry bit from the previous stage and is called Carry-in, generally represented by C_{in} . It calculates the sum of three bits along with the carry. The output carry is called Carry-out and is represented by C_{out} .

 The circuit diagram of a full adder and its truth table is given below:



TRUTH TABLE:

A	B	C	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


The i/o ports needed to be declared for the formation of full adder is given below:

Port Name	INPUT/OUTPUT	Bus
A	In	No
B	In	No
Cin	In	No
Sum	Out	No
Cout	Out	No

NB: Use temporary variable where ever necessary.

FULL ADDER USING HALF ADDERS AS COMPONENTS:

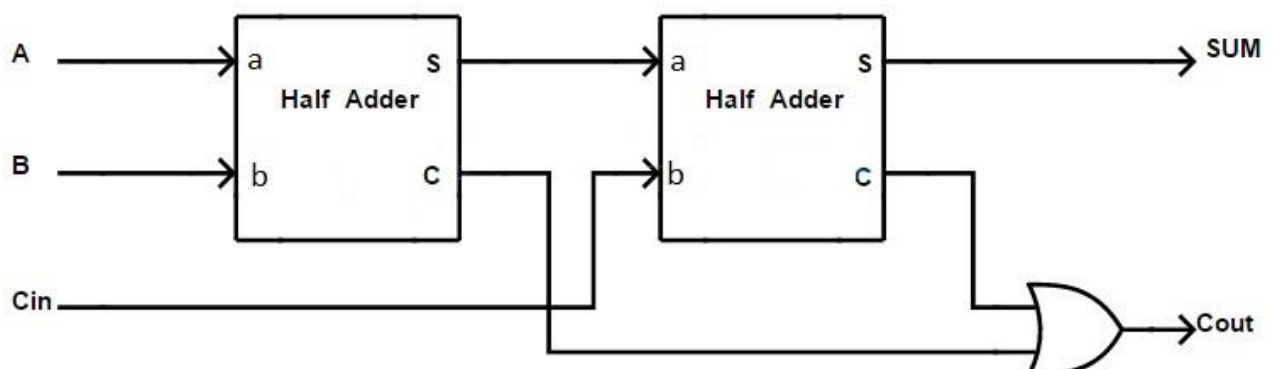The block diagram of a full adder constructed using half adder is given below:




The i/o ports needed to be declared for the formation of full adder is given below:

Port Name	INPUT/OUTPUT	Bus
A	In	No
B	In	No
Cin	In	No
Sum	Out	No
Cout	Out	No


NB: Use temporary variable where ever necessary.

How to add component and map your port from full adder to half adder

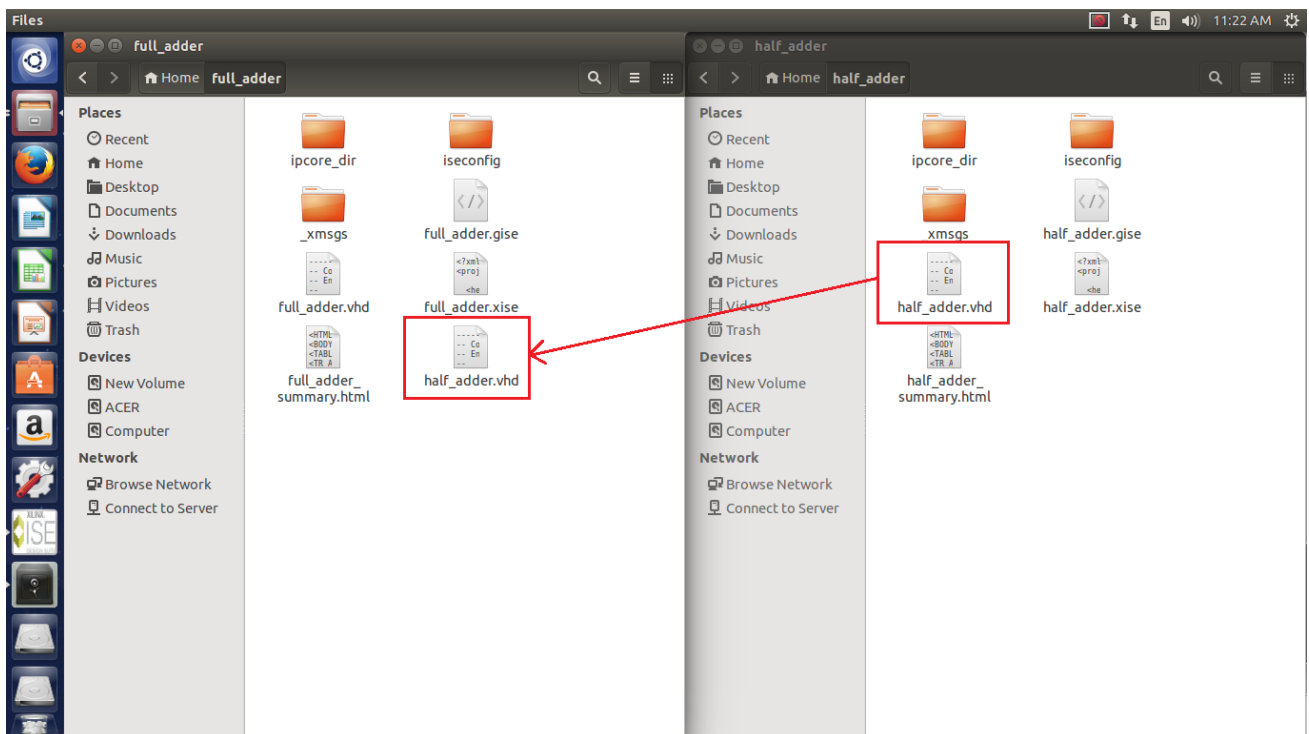Step 1: To add the half adder component, you can use the half adder **.vhd** file from your previous assignment and copy it into the full adder folder.



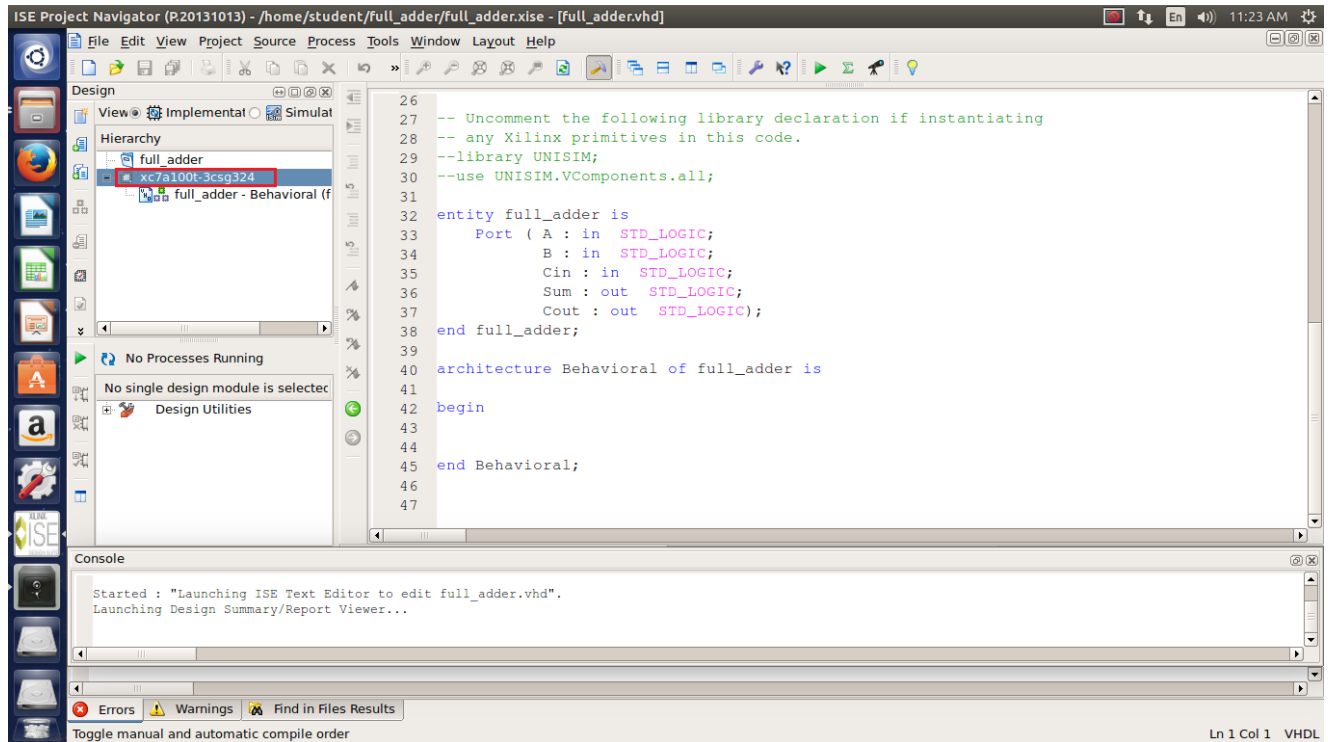Step 2: And then right click on the **parent of your full_adder-Behavioral** and select **add source**. *The place to click is marked in the image below.*




Step 3: And then browse and select your **half adder .vhd** that you copied in your full adder folder and click **open**. In the next window click **ok**.

You can also create a new vhd file for half adder if you don't have one. For that right click on the full_adder-Behavioral and click on new source and then proceed normally to create a half adder entity.

NB – Make sure that the port name for full adder and half adder are different.

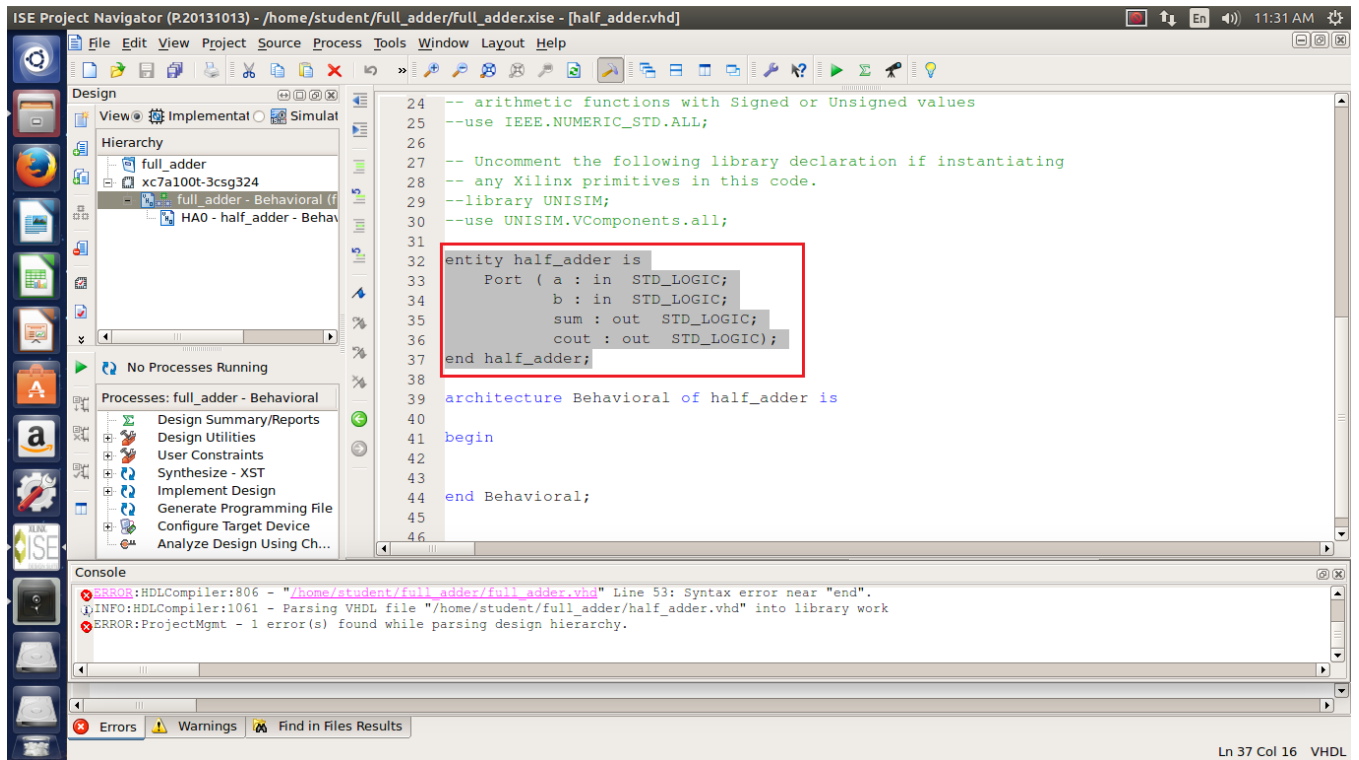Step 4: After adding the half adder .vhd file, *copy the half adder entity from the half adder's .vhd file and paste it in the behavioral block of the full adder. vhd*, as shown in the below pictures.



```

24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity half_adder is
33   Port ( a : in  STD_LOGIC;
34         b : in  STD_LOGIC;
35         sum : out STD_LOGIC;
36         cout : out STD_LOGIC);
37 end half_adder;
38
39 architecture Behavioral of half_adder is
40
41 begin
42
43 end Behavioral;
44
45
46

```


Console:

```

ERROR:HDLCompiler:806 - "/home/student/full_adder/full_adder.vhd" Line 53: Syntax error near "end".
INFO:HDLCompiler:1061 - Parsing VHDL file "/home/student/full_adder/half_adder.vhd" into library work
ERROR:ProjectMgmt - 1 error(s) found while parsing design hierarchy.

```

Ln 37 Col 16 VHDL

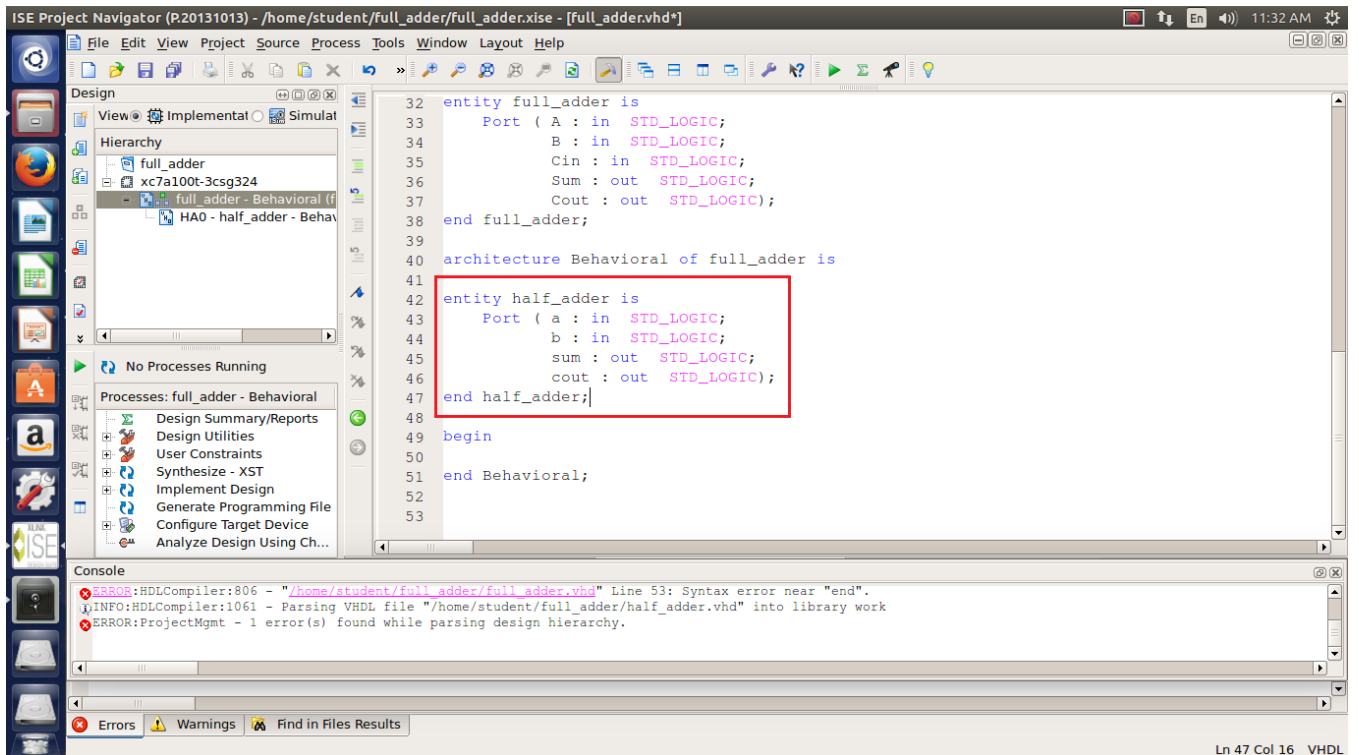

```

32 entity full_adder is
33   Port ( A : in  STD_LOGIC;
34         B : in  STD_LOGIC;
35         Cin : in  STD_LOGIC;
36         Sum : out STD_LOGIC;
37         Cout : out STD_LOGIC);
38 end full_adder;
39
40 architecture Behavioral of full_adder is
41
42 entity half_adder is
43   Port ( a : in  STD_LOGIC;
44         b : in  STD_LOGIC;
45         sum : out STD_LOGIC;
46         cout : out STD_LOGIC);
47 end half_adder;
48
49 begin
50
51 end Behavioral;
52
53

```

Console:


```

ERROR:HDLCompiler:806 - "/home/student/full_adder/full_adder.vhd" Line 53: Syntax error near "end".
INFO:HDLCompiler:1061 - Parsing VHDL file "/home/student/full_adder/half_adder.vhd" into library work
ERROR:ProjectMgmt - 1 error(s) found while parsing design hierarchy.


```

Ln 47 Col 16 VHDL

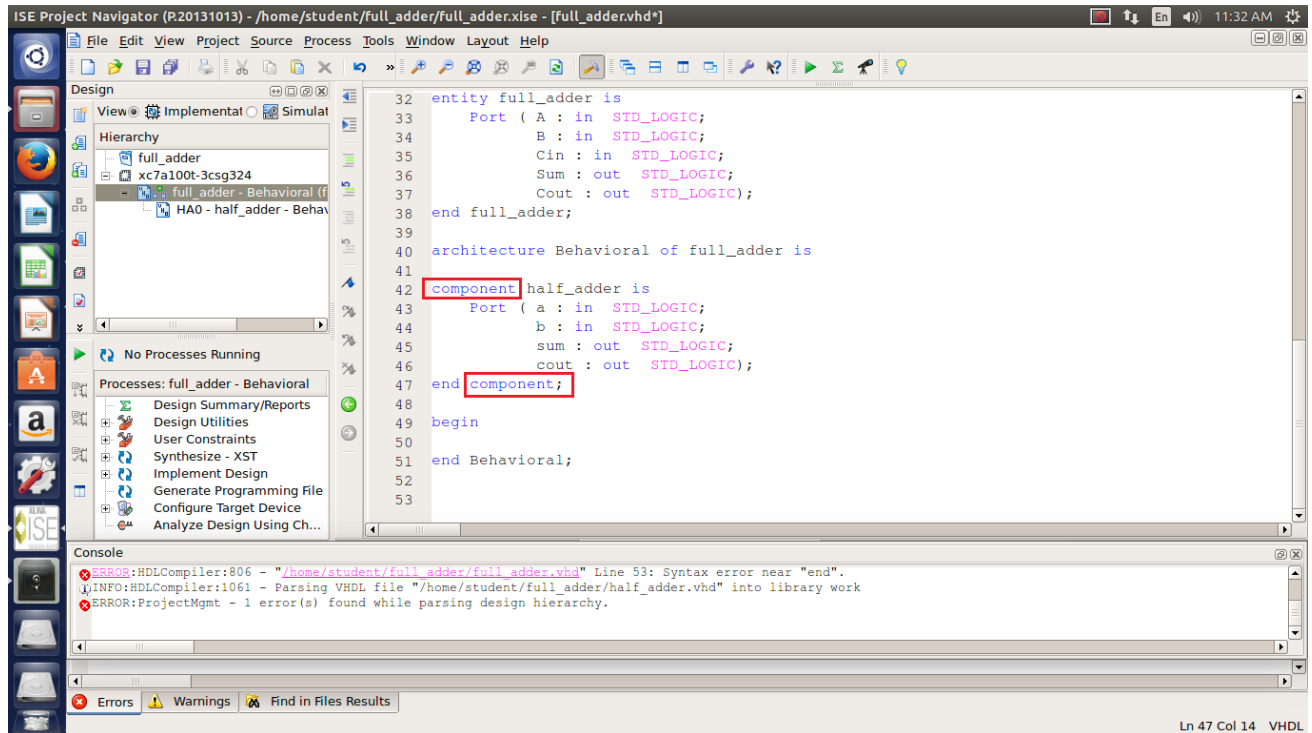Step 5: After copying the entity block make the changes marked in the image below.



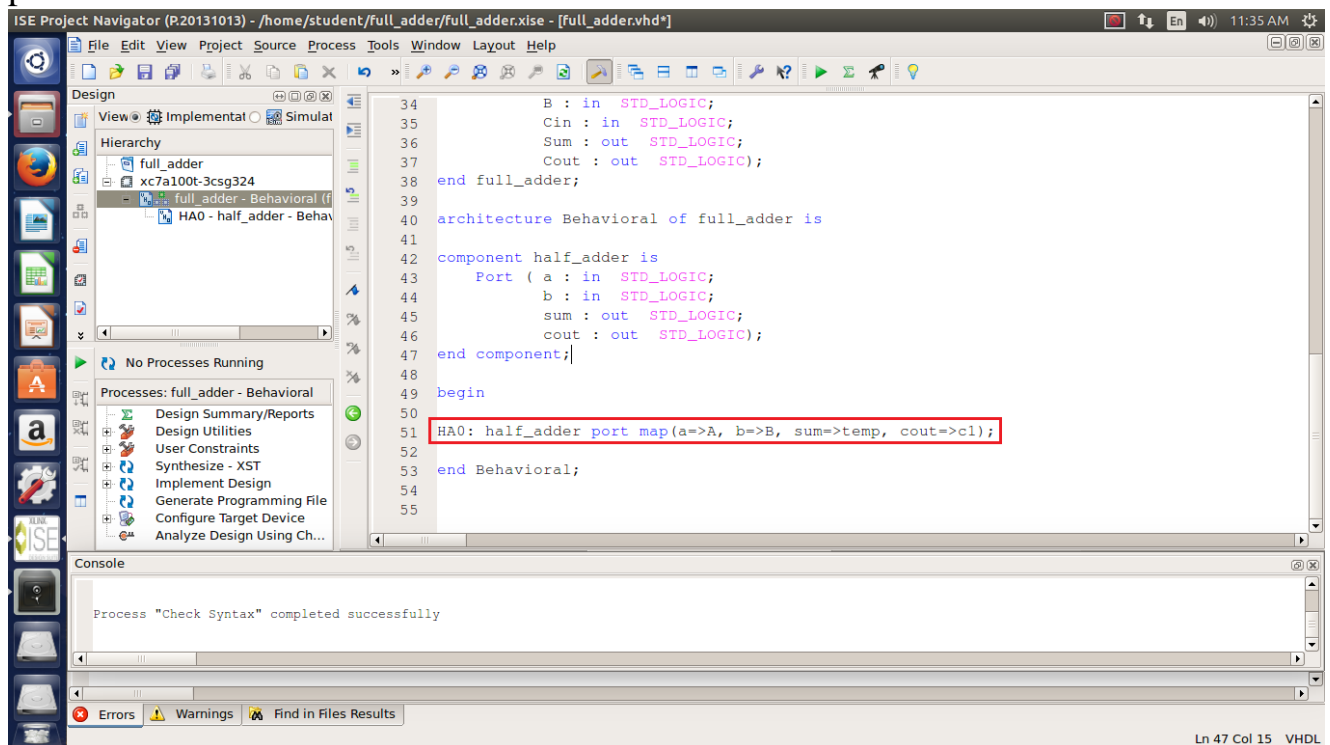Step 6: Now we need to map the ports from half adder to full adder as shown in the picture.



NB: The general syntax for port map:

Name for the port map: name_of_component port map(port_of_component=>port_of_entity)

The vhdl code for a full adder using 2 half adders will be:

entity fulladder_half is

```
Port ( A : in  STD_LOGIC;  
      B : in  STD_LOGIC;  
      Cin : in  STD_LOGIC;  
      S : out  STD_LOGIC;  
      Cout : out  STD_LOGIC);
```

end fulladder_half;

architecture Behavioral of fulladder_half is

component halfadder is

```
Port ( a : in  STD_LOGIC;  
      b : in  STD_LOGIC;  
      sum : out  STD_LOGIC;  
      c : out  STD_LOGIC);
```

end component;

```
signal temp, c1, c2 : STD_LOGIC := '0';
```

begin

```
HA0: halfadder port map(a=>A, b=>B, sum=>temp, c=>c1);
```

```
HA1: halfadder port map(a=>temp, b=>Cin, sum=>S, c=>c2);
```

```
Cout <= c1 or c2;
```

end Behavioral;